


ECEN 240 Lab 5 – Road Ripper Motor Company

Name: **Brodric Young**

Purpose:

1. To design and implement a circuit consisting of 4 inputs and 4 outputs.
2. Successfully derive a Boolean equation from a truth table using K-Maps.
3. Implement the simplified equation using a digital simulation program using gates.
4. Implement the truth table using a ROM in Logisim.
5. Implement the simplified equation using a hardware description language and a Field Programmable Gate Array (FPGA).

Project Scenario:

 

Road Ripper Motor Company

You have accepted a job with the Road Ripper Motor Company. Your first task is to upgrade the Road Ripper Motor Company's blinker and brake light system to a fully digital system.

Below is a truth table specification of what each light should do when the break is depressed (STOP input) and when the turn signal switches are activated (LEFT and RIGHT switches). The outputs are the front and rear lights on our cars.

Input (Switches)			Outputs (Lights)			
STOP	LEFT	RIGHT	L_FRONT	L_BACK	R_FRONT	R_BACK
0	0	0	0	0	0	0
0	0	1	0	0	BLINK	BLINK
0	1	0	BLINK	BLINK	0	0
0	1	1	BLINK	BLINK	BLINK	BLINK
1	0	0	0	1	0	1
1	0	1	0	1	BLINK	BLINK
1	1	0	BLINK	BLINK	0	1
1	1	1	BLINK	1	BLINK	1

0 = OFF 1 = ON BLINK = Blinking (Clocked)

In the above truth table "Blink" describes the action of the car's turn signals, but "BLINK" is not a valid logic level. To generate a signal that can turn on and off like a blinker, we can add a clock to inputs. A clock is a signal that alternates between a "1" and "0" in a periodic (repetitive) fashion. The CLOCK signal is incorporated into the modified truth table below:

Inputs				Outputs (Lights)			
STOP	LEFT	RIGHT	CLOCK	L_FRONT	L_BACK	R_FRONT	R_BACK
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	1	1
0	1	0	0	0	0	0	0
0	1	0	1	1	1	0	0
0	1	1	0	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	0	0	1	0	1
1	0	0	1	0	1	0	1
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	1
1	1	0	0	0	0	0	1
1	1	0	1	1	1	0	1
1	1	1	0	0	1	0	1
1	1	1	1	1	1	1	1

Lab 5 Part 1

Determine the Boolean equations for the brake lights and turn signals using K-Maps. Use the letters S, L, R, and C (Stop, Left, Right, and Clock) for the inputs in the Boolean expressions.

K-Maps – Complete K-map for each signal (make loops by shading with colors or patterns).

Fill out the Karnaugh map for the **left front** light:

SL \ RC		00	01	11	10
RC	00	0	0	0	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	0	0	0

Fill out the Karnaugh map for the **left back** light:

SL \ RC		00	01	11	10
RC	00	0	0	0	1
	01	0	1	1	1
	11	0	1	1	1
	10	0	0	1	1

Fill out the Karnaugh map for the **right front** light:

SL \ RC		00	01	11	10
RC	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	0	0

Fill out the Karnaugh map for the **right back** light:

SL \ RC		00	01	11	10
RC	00	0	0	1	1
	01	0	0	1	1
	11	1	1	1	1
	10	0	0	1	0

Minterm Mapping

		SL			
		00	01	11	10
RC	00	m0	m4	m12	m8
	01	m1	m5	m13	m9
	11	m3	m7	m15	m11
	10	m2	m6	m14	m10

Make sure you understand how the minterms, m0-m15, are mapped to the above K-maps. List the minterms that are present in the prime implicant loops (m0, m1, ...):

left front = $\Sigma m(\text{m5, m7, m13, m15})$

left back (loop that includes m5) = $\Sigma m(\text{m5, m7, m13, m15})$

left back (loop that includes m8) = $\Sigma m(\text{m8, m9, m10, m11})$

left back (loop that includes m14) = $\Sigma m(\text{m10, m11, m14, m15})$

right front = $\Sigma m(\text{m3, m7, m11, m15})$

right back (loop that includes m3) = $\Sigma m(\text{m3, m7, m11, m15})$

right back (loop that includes m8) = $\Sigma m(\text{m8, m9, m12, m13})$

right back (loop that includes m14) = $\Sigma m(\text{m12, m13, m14, m15})$

Boolean Reduction

What is the reduced Boolean equation for the left front light?

L_Front = **LC**

What is the reduced Boolean equation for the left back light?

L_Back = **LC + SL' + SR**

What is the reduced Boolean equation for the right front light?

R_Front = **RC**

What is the reduced Boolean equation for the right back light?

R_Back = **RC + SL + SR'**

To Verify Your Design, Take Lab 5 Quiz 1
(Quiz is worth 15 points)

Lab 5 Part 2

(You should have taken Lab 5 Quiz 1 before implementing in Logisim)

Version 1 of the Road-Ripper Circuit: Use AND, OR and NOT Gates

Implement the reduced Boolean equation in *Logisim* using AND, OR, and NOT gates. Use the following pin names:

Input Names	Output Names
Stop	L_Front
Left	L_Back
Right	R_Front
Clock	R_Back

You will find that you can simplify the Logisim circuit by noticing that one of the product terms in the L_Back signal is generated by the L_Front signal. Also, one of the product terms in the R_back signal is generated by the R_Front signal.

Make your schematic nice and neat (construction quality will affect the score you receive). Place your name under your circuit (make it large enough to read)

You should verify the circuit functionality by manually testing the input combinations shown in the original truth table.

Once you are convinced your *Logisim* implementation is correct, demonstrate its functionality using the “test vector” tool available in *Logisim Evolution*.

- Download the test file called “Road_Ripper_test.txt” found in the Lab3 module in *I-Learn*.
- Place the file in your *Logisim Evolution* folder.
- Run the “Test Vector” tool from the “Simulate” menu of *Logisim Evolution*.
- Select “Load Vector” and navigate to the “Road_Ripper_test” file.
- The tool will display a truth table showing the tests that passed and the tests that failed. Keep working on your circuit until there are no failures.
- Take a “snapshot” of the window showing your test results, and paste the snapshot in the submission box below:

(The “test vector” border box will expand to fit a screen-shot of your test results)


Passed: 16 Failed: 0									
Status	Stop	Left	Right	Clock	L_Front	L_Back	R_Front	R_Back	
pass	0	0	0	0	0	0	0	0	
pass	0	0	0	1	0	0	0	0	
pass	0	0	1	0	0	0	0	0	
pass	0	0	1	1	0	0	1	1	
pass	0	1	0	0	0	0	0	0	
pass	0	1	0	1	1	1	0	0	
pass	0	1	1	0	0	0	0	0	
pass	0	1	1	1	1	1	1	1	
pass	1	0	0	0	0	1	0	1	
pass	1	0	0	1	0	1	0	1	
pass	1	0	1	0	0	1	0	0	
pass	1	0	1	1	0	1	1	1	
pass	1	1	0	0	0	0	0	1	
pass	1	1	0	1	1	1	0	1	
pass	1	1	1	0	0	1	0	1	
pass	1	1	1	1	1	1	1	1	

Load Vector
Run
Stop
Reset
Close Window

Road Ripper Test Vector Results with “AND, OR, NOT” Gates (10 points)

Take a “snapshot” of the circuit (including your name), and paste the snapshot in the submission box below:

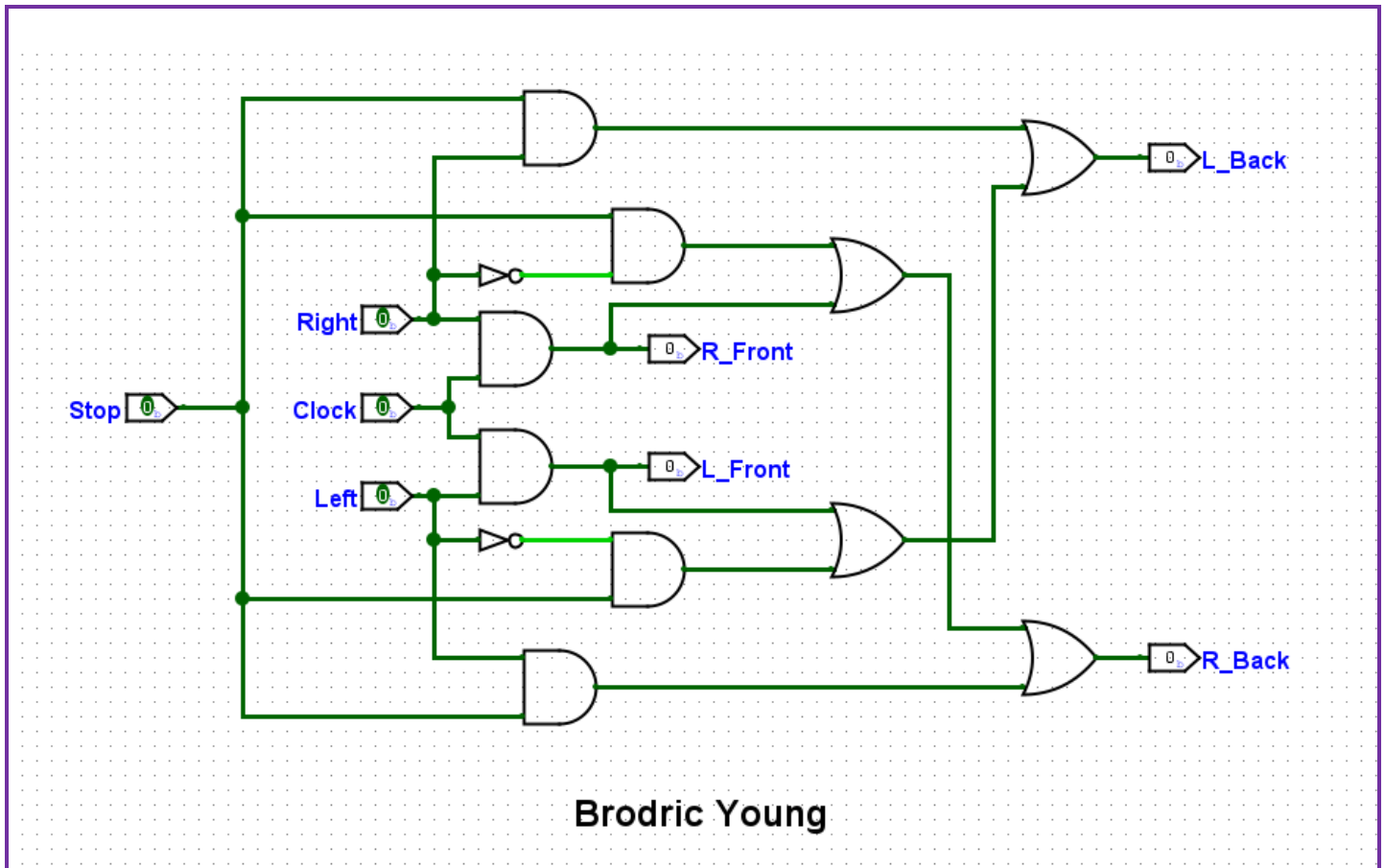(The circuit box should expand to fit the size of your screen-shot)



Logisim Evolution Circuit with “AND, OR, NOT” Gates (10 points)


Version 2 of the Road-Ripper Circuit: Use a ROM to build the circuit

Implement the reduced Boolean equation in *Logisim* using a ROM (Use a single ROM and no other gates). A ROM (Read Only Memory) acts very much like a truth table, so the entire truth table may be entered into the ROM.

The *Logisim* ROM is found in the "Memory" folder. The address bit width should be set to 4 bits (each address bit serving as one of four input signals). The data bit width will also be set to 4 bits (each data bit serving as one of the four output signals):

Properties	Registers
Selection: ROM	
VHDL	Verilog
Address Bit Width	4
Data Bit Width	4
Contents	(click to edit)
Label	HDL Required
Label Font	SansSerif Bold 16
Label Visible	No

 A ROM with 4 address bits has 2^4 memory locations, and each memory location in this ROM is set to store 4 bits. The *Logisim Evolution* symbol for the ROM looks like this:




Notice that the ROM Address input is at the upper left of the symbol, and it appears that all 4 address bits are merged into a single wire “bundle”. This is called a “bus” and makes schematic diagrams easier to read. The “Data” output is at the bottom right of the symbol, and all four outputs are merged into a single bus, as well. To access each wire in a bus, you will need to use a “splitter” from the wiring menu of *Logisim*.

Place a splitter in your circuit, and set the options to:


Properties	
Registers	
Selection: Splitter	
VHDL	Verilog
Facing	West
Fan Out	4
Bit Width In	4
Appearance	Left-handed
Bit 0	0 (Top)
Bit 1	1
Bit 2	2
Bit 3	3 (Bottom)

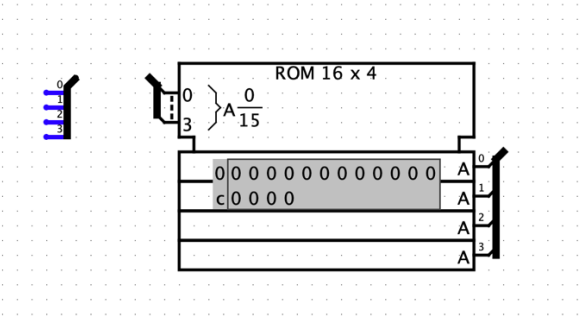Move the splitter into position as shown:



The “0” on the splitter represents the Least Significant Bit (LSB) and the “3” on the splitter represents the Most Significant Bit (MSB). The LSB corresponds to the “Clock” signal (C), and the MSB corresponds to the “Stop” signal (S).

Connect the respective signals as shown:

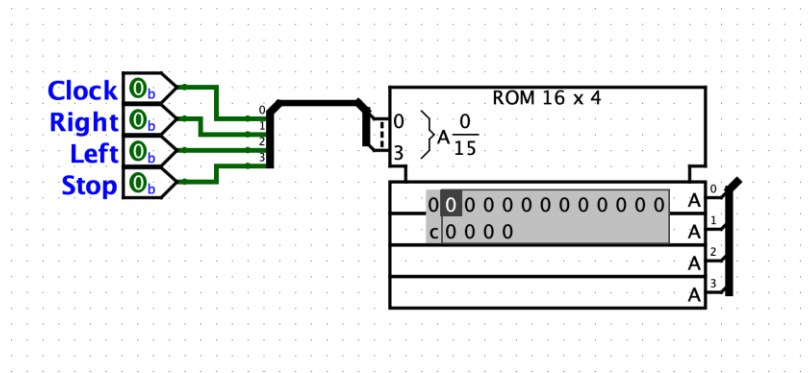

To connect the outputs, you will need the splitter to be oriented “West” instead of “East”.

Remember to connect the output signals to the proper splitter pin, and add your name below the ROM circuit.

By default, there is no data stored in memory. There are a couple of ways to program Logisim ROMs. One way is to use the poke tool (the hand with the index finger extended). Select the poke tool, select the ROM, then select the cell you want to edit and type a hexadecimal value. The other way to edit the contents of the ROM is to select the ROM with the edit tool and then in the “Selection: ROM” window, click the “(click to edit)” item in the “Contents” row of the window. This pops up a “Logisim: Hex Editor” window. Select the cell you want to edit in the Hex Editor and enter a hexadecimal value. You can save the contents of the hex editor to a file and open files from which you can read into the hex editor.

The value in using a ROM to implement your truth table is that there is no need for simplification. Simply enter the output data from the truth table into the proper address location!

You should verify the circuit functionality by manually testing the input combinations shown in the original truth table.

Once you are convinced your *Logisim* implementation is correct, demonstrate its functionality using the same test vector file you used for the AND, OR, NOT implementation. Paste a snapshot of the results below:


(The “test vector” border box will expand to fit a screen-shot of your test results)

Passed: 16 Failed: 0									
Status	Stop	Left	Right	Clock	L_Front	L_Back	R_Front	R_Back	
pass	0	0	0	0	0	0	0	0	
pass	0	0	0	1	0	0	0	0	
pass	0	0	1	0	0	0	0	0	
pass	0	0	1	1	0	0	1	1	
pass	0	1	0	0	0	0	0	0	
pass	0	1	0	1	1	1	0	0	
pass	0	1	1	0	0	0	0	0	
pass	0	1	1	1	1	1	1	1	
pass	1	0	0	0	0	1	0	1	
pass	1	0	0	1	0	1	0	1	
pass	1	0	1	0	0	1	0	0	
pass	1	0	1	1	0	1	1	1	
pass	1	1	0	0	0	0	0	1	
pass	1	1	0	1	1	1	0	1	
pass	1	1	1	0	0	1	0	1	
pass	1	1	1	1	1	1	1	1	

Road Ripper Test Vector Results with ROM (10 points)

Take a “snapshot” of the circuit (including your name), and paste the snapshot in the submission box below:

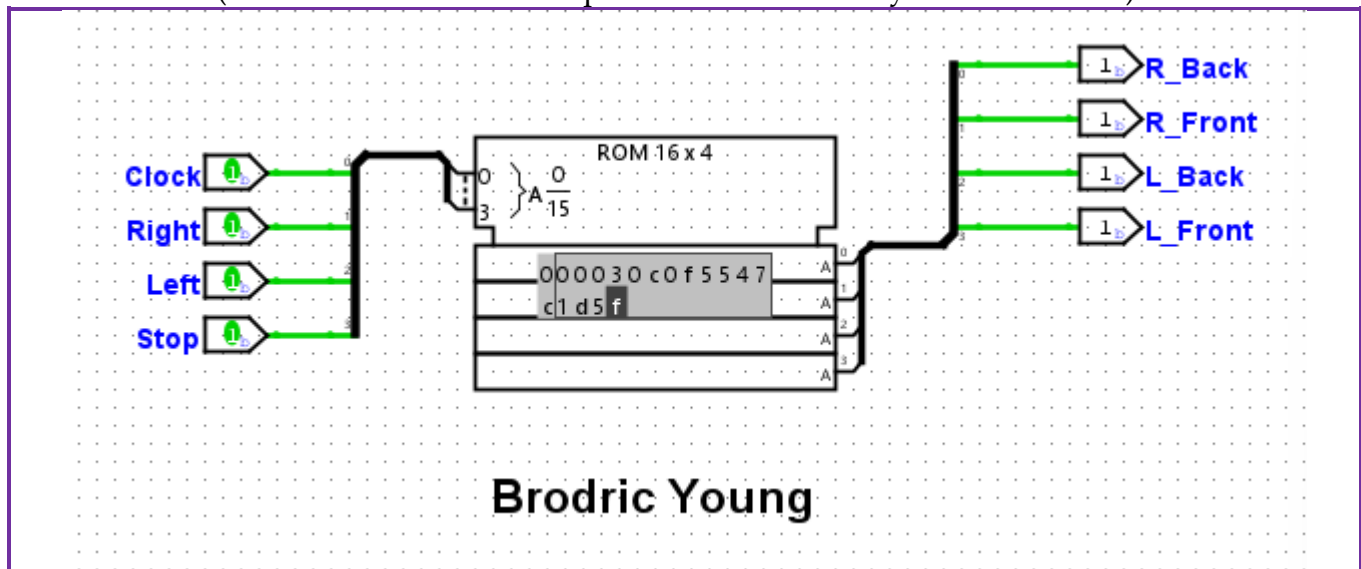(The circuit box should expand to fit the size of your screen-shot)




Logisim Evolution Circuit with ROM (10 points)

Lab 5 Part 3

Vivado Tutorial

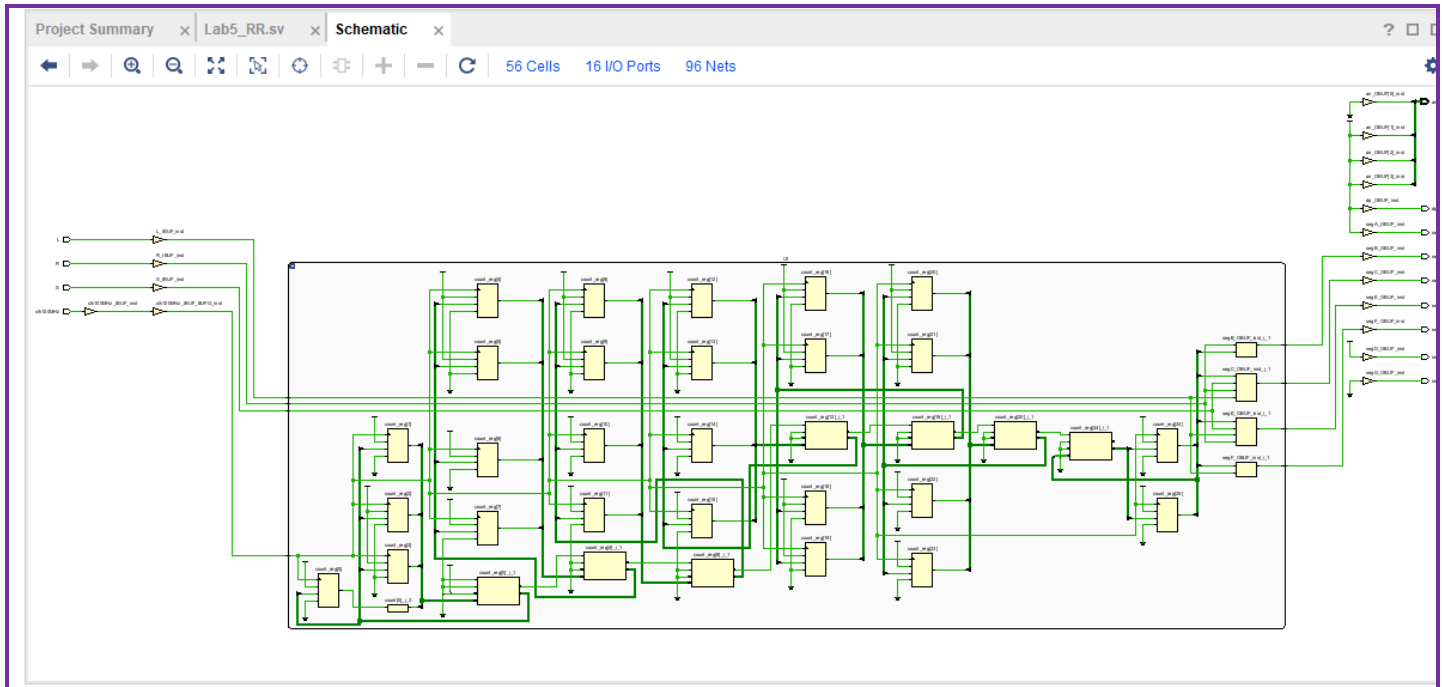Complete the Vivado Tutorial (instruction document found in the module for this lab).



Screenshot of the elaborated design schematic (10 points)

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 02/12/2021 07:33:11 AM
// Design Name:
// Module Name: Lab5_RR
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
```

```
//
////////////////////////////////////

module Lab5_RR_top(
    input logic S,
    input logic L,
    input logic R,
    input logic clk100MHz,
    output logic [3:0] an,
    output logic segA, segB, segC, segD, segE, segF, segG,
    output logic dp
);

    logic clk;
    logic LF, LB, RF, RB;

    Lab5_RR U0 (S, L, R, clk, LF, LB, RF, RB);
    clk_gen U1 (clk100MHz, clk);

    assign an = 4'b1110; // 1110 only turns on the Right 7-segment display
    assign dp = 1'b1; // a logic 1 means off
    assign segA = 1'b1; // a logic 1 means off
    assign segB = !RF;
    assign segC = !RB;
    assign segD = 1'b1;
    assign segE = !LB;
    assign segF = !LF;
    assign segG = 1'b0; // Turn on the middle segment to represent the car

endmodule

module Lab5_RR(
    input logic Stop,
    input logic Left,
    input logic Right,
    input logic Clock,
    output logic L_Front,
    output logic L_Back,
    output logic R_Front,
    output logic R_Back
);
    logic in_Left, in_Right, Stop_Left, Stop_Right, Stop_inRight, Stop_inLeft; //put your list of
    internal signals here

```

```

not (in_Left, Left);
not (in_Right, Right);

and (Stop_inLeft, in_Left, Stop);
and (Stop_Left, Stop, Left);
and (L_Front, Left, Clock);
and (R_Front, Clock, Right);
and (Stop_Right, Stop, Right);
and (Stop_inRight, Stop, in_Right);

or (L_Back, L_Front, Stop_inLeft, Stop_Right);
or (R_Back, R_Front, Stop_inRight, Stop_Left);
endmodule

module clk_gen(
    input logic clk100MHz,
    output logic clk
);

    logic [25:0] count;

    assign clk = count[25];
    always_ff @(posedge clk100MHz)
        count <= count + 1;
endmodule

```

Your SystemVerilog module code (10 points)

To Pass off your design, take Lab 5 Quiz 2
(Quiz is worth 10 points)

Conclusions Statement

Write a brief conclusions statement that discusses the original purposes of the lab found at the beginning of this lab document.

- What are the difficulties related to designing a 4-input, 4-output circuit?
- What are your thoughts on using K-maps VS Boolean Equations to simplify logic problem?
- Compare implementing a circuit with logic gates to implementing a circuit with a programmable logic device (like a ROM).
- Describe your first impressions about using SystemVerilog to program an FPGA in the Vivado Environment. How does this compare with building your circuit on a breadboard?

Please use complete sentences and correct grammar to express your thoughts:

(The conclusions box will expand as you write)

Through this lab, I found some difficulties related to designing a 4-input, 4-output circuit. One is that the schematic can get a little messy and confusing when using logic gates. It usually takes a lot of gates and wires going everywhere with multiple inputs and outputs. It definitely helps simplify the schematic by simplifying the equations beforehand, whether with K-maps or Boolean equations. Boolean equations aren't too bad for short simple equations or if there's more than 4 inputs but for equations with many terms or 4 or less inputs it seems K-maps make it really easy to simplify. Also in this lab, we implemented a circuit using logic gates and then with a ROM. Our specific circuit wasn't too bad to create using logic gates, but as you keep getting bigger and more complex equations using a ROM gets easier and easier to use because you just set what the output should be for a given input combination. We also used SystemVerilog to program a FPGA instead of building the circuit on a breadboard. My first impressions of SystemVerilog was that it will take some practice and experience to learn how to use it and to program everything myself but in the end it will be a lot easier than building it myself on a breadboard. The FPGA does the same thing it would on a breadboard, but the difference is that we program the FPGA and tell it how to build the circuit and it builds it for us.

Conclusions Statement (15 points)

Congratulations, you have completed the lab!

You may now submit this document.