

ECEN 240 - Lab 8 – Sequential Circuits – Latches and Flip Flops

Name: **Brodric Young**

Purposes:

1. Become familiar with:
 - SR (SC) Latches
 - Gated D Latches
 - D Flip Flops
2. Be able to read and implement transition tables for latches
3. Build D Flip Flops in SystemVerilog
4. Learn how to implement flip flops using SystemVerilog

Procedure:

This lab uses *Logisim Evolution* to simulate latches and Flip Flops, and then implements the Flip Flop circuits in SystemVerilog.

This lab uses *Logisim Evolution* to simulate memory elements (latches and flip-flops), then SystemVerilog is used to build the flip flop circuits.

- In part 1 you will simulate three different latch circuits all in one *Logisim* file. Keep the latch circuits in one file so you can more easily compare their behavior.
- In part 2 you will simulate a D flip flop circuit and a D flip flop toggle circuit. You should build these two circuits in one file.
- In part 3 the flip flop circuits will be built using SystemVerilog.

Part 1 – Latches and Gated latches

NOR SR Latches

The S and R signals of a NOR-based latch are normally set to “0”. One of the two signals must transition from low-high in order for something to change at the outputs. You can better understand the meaning of this transition table if you let the high-going pulse be substituted for the “1” in section 15.1 of the textbook, suggesting that Q takes on the value of $Q+$ as the appropriate S or R signal transitions from 0 to 1. The latch retains its value even after transitioning back to its normal value of “0”.

The NOR-based latch circuit of figure 15.1 of the textbook results in the truth (or transition) table shown below (compare with figure 15.4 of the textbook):

NOR-Based SR Latch							
Inputs (for brevity, Q' not shown)			Expected Next State of Q and Q'		Simulated Next State of Q and Q'		
S	R	Q	Q ₊	Q' ₊	Q ₊	Q' ₊	Q' ₊
0	0	0	0	1	0	1	1
0	0	1	1	0	1	0	0
0	⌋	0	0	1	0	1	1
0	⌋	1	0	1	0	1	1
⌋	0	0	1	0	1	0	0
⌋	0	1	1	0	1	0	0
1	1	0	NA	NA	0	0	0
1	1	1	NA	NA	0	0	0

For the invalid input conditions in the above table, *NA* means “Not Allowed”.

Build the NOR latch circuit in *Logisim*, simulate the circuit, and record your results in the “Simulated Next State” column of the above table. This time, use the actual simulated values of the outputs for all cases (don’t use *NA*).

Use the following pin names in your *Logisim* circuit:


Input Pins	Output Pins
S_NOR	Q_NOR
R_NOR	Qn_NOR

Note that you will not be able to test latches and flip flops like you did combinational logic (where you might have gone sequentially through each line of the truth table). The output is not just dependent on the setting of the inputs. The output is dependent on the state of the inputs and the previous state of the output. You will need to do some extra input manipulation (setting or clearing the latch or flip flop) to get the *Q* output to what it needs to be to test a particular input condition.

You can verify the signals are connected correctly by testing your circuit with the “NOR_Latch_test.txt” test vector file, but there is no need to submit the results until all three latches are constructed.

NAND S'R' Latches

 The NAND latch isn’t discussed in the textbook, but it is simple to draw the NAND latch from the NOR latch schematic. Simply replace the NOR gates with NAND gates, change the *S*, *R* signals to *S'* and *R'*, and swap the *Q* and *Q'* outputs as shown:



The NAND latch input signals are complemented relative to the NOR latch. The *S'* and *R'*

signals of the NAND-based latch are normally set to “1”. One of the two signals must transition from high-low in order for something to change at the outputs. You can better understand the meaning of the NAND latch transition table if you let low-going pulse be substituted for the “0” in the transition table, suggesting that Q takes on the value of $Q+$ as the appropriate S' or R' signal transitions from 1 to 0. The latch retains its value even after transitioning back to its normal value of “1”.

Before you build the NAND latch, predict the expected next states of the outputs and fill out the “Expected Next State” column of the table below (don’t fill out the “Simulated” column yet):

NAND-Based S'R' Latch							
Inputs (for brevity, Q' not shown)			Expected Next State of Q and Q'		Simulated Next State of Q and Q'		
S_{not}	R_{not}	Q		$Q+$	$Q'+$		
0	0	0		NA	NA		
0	0	1		NA	NA		
$\overline{\text{U}}$	1	0		0	1		
$\overline{\text{U}}$	1	1		0	1		
1	$\overline{\text{U}}$	0		1	0		
1	$\overline{\text{U}}$	1		1	0		
1	1	0		1	1		
1	1	1		1	1		

For the invalid input conditions in the above table, NA means “Not Allowed”.

After you predict the expected outputs, build the NAND latch circuit in the same *Logisim* circuit file as the NOR latch (there is no need to build sub-circuits). Simulate the circuit and record your simulated results in the “Simulated Next State” column of the above table (use the actual simulated values of the outputs for all cases, don’t use NA).

Use the following pin names in your *Logisim* circuit:

Input Pins	Output Pins
$S_{\text{n_NAND}}$	Q_{NAND}
$R_{\text{n_NAND}}$	$Q_{\text{n_NAND}}$





Remember that you will need to do some extra "button clicking" to get the Q output to the proper state on the input side of the transition table.

You can verify the signals are connected correctly by testing your circuit with the “NAND_Latch_test.txt” test vector file, but there is no need to submit the results until all three latches are constructed.

Gated D Latches

Consider the Gated of Figure 15.7 of the textbook. The S and R inputs are replaced by a single D input. The inverter eliminates any states that are “Not Allowed”. The *Gate* signal is normally set to “0” and must transition from low-high in order for something to change at the outputs. You can better understand the meaning of this transition table if you let the high-going pulse be substituted for the “1” in Figure 15.9 of the textbook, suggesting that Q takes on the value of D as the *Gate* signal transitions from 0 to 1. The latch retains its value even after transitioning the *Gate* back to its normal value of 0.

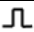Before you build the Gated D latch, predict the expected next states of the outputs (by looking at the circuit in 15.7 of the textbook) and fill out the “Expected Next State” column of the table below (don’t fill out the “Simulated” column yet):

Gated D-Latch							
Inputs (for brevity, Q' not shown)			Expected “Next State” of Q and Q'		Simulated “Next State” of Q and Q'		
Gate	D	Q		Q_+	Q'_+		Q_+ Q'_+
0	0	0		0	1		0 1
0	0	1		1	0		1 0
0	1	0		0	1		0 1
0	1	1		1	0		1 0
	0	0		0	1		0 1
	0	1		0	1		0 1
	1	0		1	0		1 0
	1	1		1	0		1 0

After you predict the expected outputs, build the NAND latch circuit in the same *Logisim* circuit file as the NOR latch (there is no need to build sub-circuits). Simulate the circuit, and record your results in the “Simulated Next State” column of the table. Use the actual simulated values of the outputs for all cases (don’t use *NA*). Use the following pin names in your *Logisim* circuit:

Input Pins	Output Pins
Gate	Q_GateD
D	Qn_GateD

Remember that you will need to do some extra “button clicking” to get the Q output to what it needs to be to test a particular input condition.

You can verify the signals are connected correctly by testing your circuit with the “Gated_DLatch_test.txt” test vector file.

Test your three latches together using the “Latches_test.txt” test vector file, and paste your results in the box below:

Test Vector main of Lab8_Latches_and_FlipFlops

Passed: 6 Failed: 0


Status	S_NOR	R_NOR	Sn_NAND	Rn_NAND	Gate	D	Q_NOR	Qn_NOR	Q_NAND	Qn_NAND	Qn_GateD	Q_GateD
pass	0	1	0	0	1	0	0	1	1	1	1	0
pass	0	1	0	0	1	0	0	1	1	1	1	0
pass	1	0	0	1	1	1	1	0	1	0	0	1
pass	1	0	0	1	1	1	1	0	1	0	0	1
pass	1	1	1	0	1	0	0	0	0	1	1	0
pass	1	1	1	0	1	1	0	0	0	1	0	1

Buttons: Load Vector, Run, Stop, Reset, Close Window


Paste your *Logisim* circuit (including your name) in the box below. Remember, this design will have all 3 latches (without subcircuits):

Brodrick Young


NOR Latch

 

NAND Latch

 

Gated D Latch

 

Three-Latch *Logisim* Circuit (10 points)

***** Take Lab8 Quiz 1 *****
(Worth 20 points)

Part 2 – Flip Flops


D Flip Flop Circuit

Consider Figures 15.17 and 15.18 in the textbook to predict the expected transition data for a rising edge triggered Flip Flop. Enter in your “Expected Next State” data in the table below (don’t enter the “Simulated Next State” data yet).

D Flip Flop					
Inputs (for brevity, Q' not shown)			Expected Next State of Q and Q'		
CLK	D	Q	Q+	Q'+	
↑	0	0	0	1	
↑	0	1	0	1	
↑	1	0	1	0	
↑	1	1	1	0	

In this half of the lab, you will create a new *Logisim* file. You won’t need to build your own D flip flop out of AND, OR, and NOT gates! In *Logisim*, the *D Flip-Flop* is found in the "Memory" folder. To verify the behavior of the D FF, *Logisim* does not require that you connect the *S* and *R* pins. Leave them disconnected for now.

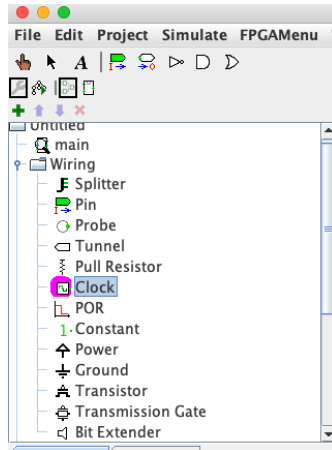- Connect the clock input (the input with the triangle) to a clock source from the wiring menu, and name the clock pin “*clk*”:



- Connect the *D* input of the flip flop to a regular input pin and call this signal, “*D*”.
- Connect the output pins, *Q* and *Q'* to regular output pins called “*Q*” and “*Qn*”.

The clock pin is unique in Logisim because it is capable of automatically cycling through the 1-0-1-0... sequence at the frequency you specify! Go to the “Simulate -> Tick Frequency” menu to set the frequency. Pick a frequency like 1Hz (1 cycle per second). Alter this frequency as desired. To start the clock, select “Simulate -> Ticks Enabled”. If you don’t want the clock to “free run”, simply turn it off, and use the poke tool (the finger) to change the clock state just like any other input pin.


Do the following tests on the flip flop circuit:

- With your clock “free running” at 1Hz, observe what happens when you change the *D* input from 0 to 1 and back again.
- With the *D* input set to 1 and the clock running at 1Hz, observe what happens when you connect the *R* input of the flip flop to an input pin and manipulate its value from 0-1-0-1....

- With the D input set to 0, R set to 0, and the clock running at 1Hz, observe what happens when you connect the S input of the flip flop to an input pin and manipulate its value from 0-1-0-1...
- Observe what happens when you simultaneously set the R and S pins to 1 (which one wins?).


D Flip Flop Toggle Circuit

 In the same *Logisim* circuit file as the *D flip flop* circuit, construct a toggle circuit using a *D* flip flop in Logisim and examine its behavior. Section 15.3 of the textbook shows such a circuit:




Note that the above circuit uses a negative edge triggered *D flip flop*. For your implementation, use the positive edge triggered Logisim *D flip flop* instead. Also, the circuit shows an inverter connected from the Q output to the D input. You can simply use the Q' output without the inverter.

 Verify that the toggle circuit behaves as shown in the timing diagram:




This toggle circuit divides a frequency by 2. In other words, the frequency seen at the Q output is half that seen at the clock input.

 Logisim Evolution has the capability of showing you a timing diagram similar to the one above. To do this, we'll modify your circuit above to look like this:



STEPS


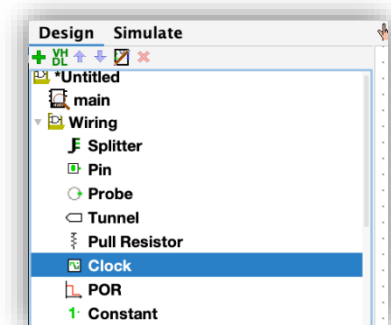
1. Make sure you've used a positive-edge FF from the Library: **Memory/D Flip-Flop**
2. We want to add a clocking element from the Wiring menu → **Wiring/Clock**
3. Label the Clock Element "**CLK**". Make sure you have an output labelled "**Q**" as shown.
4. Add an outbound pin to the D of the FF and label it "**D**". Note that this is an output because the FF is driving it back through the Inverter.




We label the wires of interest so that they are available to show up on the Timing diagram too.

5. Open the Timing Diagram tool from the Simulate menu →


6. Click the “Add or Remove Signals”

 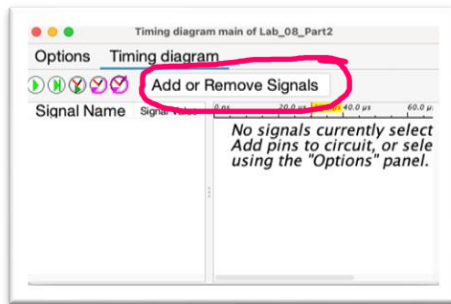

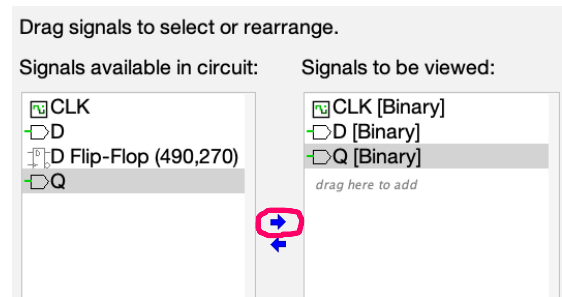
7. Add the three signals, **CLK, D, Q** →



 8. Go to the “Timing Diagram” and use the round clocking buttons to advance the timing diagram plotting from one of the control button: continuously, step-by-step, a half-clock, or full-clock cycle.



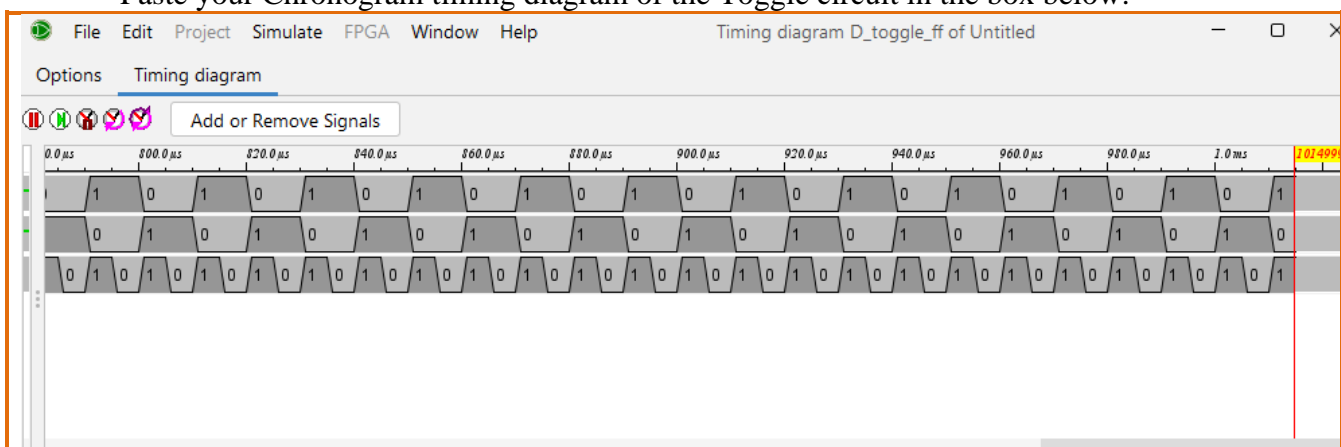Paste your Chronogram timing diagram of the Toggle circuit in the box below:




Timing Diagram of the Toggle Circuit (10 points)


Paste your *Logisim* circuit of your flip flop and toggle circuit (including your name) in the box below:

Brodrick Young

Flip Flop

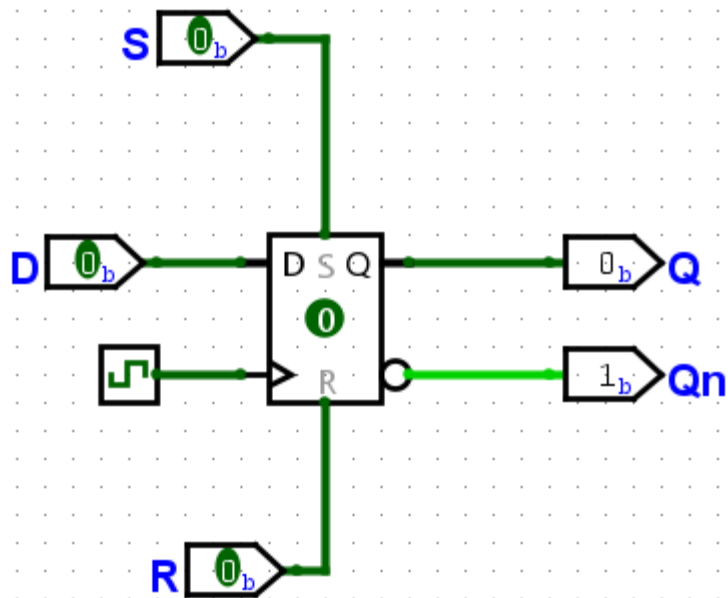

Toggle Circuit

 

Flip Flop Circuits (10 points)

Take Lab8 Quiz 2

(Worth 10 points)

Part 3 – SystemVerilog Flip Flops

SystemVerilog Flip Flops

Refer to the SystemVerilog instruction document to implement the flip flop circuits on a Basys3 board.

Paste your module that contains the flip flop “always_ff” statement in the box below:

```
always_ff @ (posedge clk_slow) // This is our flip flop
begin
    ALU_out_FF <= ALU_out; // It takes the ALU_out and then puts it through the flip flop and
                           // outputs the result in ALU-out_FF
end // it ends here then runs again since its an always loop
```

Flip Flop Module Code (10 points)

*****Pass Off the Flip Flop Implementation Using Lab8 Quiz 3*****
(Worth 10 points)

Conclusions Statement

Write a brief conclusions statement that discusses the original purposes of the lab found at the beginning of this lab document.

- What are some of your observations about: SR Latches, Gated D Latches, and D Flip Flops?
- What are some of your observations about reading and implementing transition tables?
- What are your observations about implementing flip flops behaviorally in SystemVerilog?

Please use complete sentences and correct grammar to express your thoughts:

(The conclusions box will expand as you write)

In this lab we made a flip flop both in Logisim and programmed into the FPGA. These flip flops can be made with SR latches or gated D latches. The latches can hold onto data, being set or reset but holding onto the data until then but the gated one has a gate on it that only lets the data change when the gate is on. So it would seem like gated d latches are safer and easier only using one input, but SR latches are faster and use less gates. To implement our flip flop, we read and implemented transition tables which was similar to truth tables but a little different. These also depended on the initial state of Q and the other inputs and was less simple to test because it needed a few extra clicks to get the setup right. To actually implement the flip flop in SystemVerilog was easier than I expected. Setting everything up was a little difficult but the code for the flip flop itself was surprisingly simple.

Conclusions Statement (10 points)

Congratulations, you have completed the lab!

You may now submit this document.